

EE2016 Experiment 2

Group 3 - EE23B039, EE23B033, EE23B027

1 Aim:

To display the outputs of a 3 bit johnson counter on a 7 segment display on FPGA board

2 D Flip Flop without Reset

Code for Module

```
//circuit D Flipflop

module d_flipflop(q, q_bar, d, clk);
    output reg q, q_bar;
    input d, clk;
    always @(posedge clk)
    begin
        q <= d;
        q_bar = ~q;
    end
endmodule
```

Testbench

```
// testbench for d_flipflop
`timescale 1ns/100ps

module test_dff;
    wire q, q_bar;
    reg d, clk;

    initial begin
        clk = 0;
        forever
            #10
            clk = ~clk;
        end

    d_flipflop DUT(q, q_bar, d, clk);

    initial begin

        $dumpfile("d_flip_flop.vcd");
        $dumpvars(0, test_dff);
        d = 0;
        #10
        d = 1;
        #10
        d = 0;
        #100
        $finish;

    end

endmodule
```

3 D Flip Flop with Reset

Code for Module

```
//circuit d_flip_flop_with_reset

module dflipflop_with_reset(q, q_bar, d, rst, clk);
    output q, q_bar;
    input d, rst, clk;
    reg q, q_bar;

    always @ ( posedge clk)
    begin
        if (~rst)
        begin
            q <= 1'b0;
            q_bar <= 1'b1;
        end

        else
        begin
            q <= d;
            q_bar <= ~q;
        end
        //q_bar = ~q;
    end

endmodule
```

Testbench

```
// testbench for d_flipflop
`timescale 1ns/100ps

module test_dff_rst;
    wire q, q_bar;
    reg d, clk, rst;

    initial begin
        clk = 0;
        forever
            #10
            clk = ~clk;
        end

    dflipflop_with_reset DUT(q, q_bar, d, rst, clk);

    initial begin

        $dumpfile("d_flip_flop_rst.vcd");
        $dumpvars(0, test_dff_rst);
        // Initial conditions
        rst = 1;
        d = 0;

        // Apply stimulus
        #10 rst = 1; d = 1;
        #10 rst = 0; d = 1;
        #10 rst = 0; d = 0;
        #10 rst = 1; d = 1;

        // End simulation
        #50
    end
endmodule
```

```

    $finish;
end

```

```
endmodule
```

4 3-bit Johnson Counter

Code for Module

```

//Johnson counter

module johnson_counter(out, clk, rst);
    output reg[2:0] out;
    input clk, rst;
    wire q2, q1, q0, q2b, q1b, q0b;

    dfflipflop-with-reset d2(q2, q2b, q0b, rst, clk);
    dfflipflop-with-reset d1(q1, q1b, q2, rst, clk);
    dfflipflop-with-reset d0(q0, q0b, q1, rst, clk);

    always @(posedge clk)
        begin
            if (~rst)
                begin
                    out <= 3'b000;
                end
            else
                begin
                    out <= {q2, q1, q0};
                end
            end
        end

endmodule

```

Testbench

```

//testbench johnson_counter

`timescale 1ns/100ps

module test_johnson_counter;
    wire[2:0] out;
    reg clk, rst;
    reg q2, q1, q0, q2b, q1b, q0b;

    initial begin
        clk = 0;
        forever
            #10
            clk = ~clk;
        end

    johnson_counter DUT(out, clk, rst);

    initial begin
        $monitor("At t=%t, out=%b", $time, out);
        rst = 0;
        #10
        rst = 1;
        #10
        rst = 0;
        #10
        rst = 1;
    end
endmodule

```

```

                                #100
                                $finish;
                                end
endmodule

```

5 Clock Divider

Code for Module

```

module clk_divider(inClk,reset,outClk);
    input inClk;
    input reset;
    output outClk;
    reg outClk;
    reg[32:0] clockCount;

    always @(posedge inClk)
        begin
            if (reset == 1'b0)
                begin
                    clockCount <= 33'b0;
                    outClk <= 1'b0;
                end

            else
                begin
                    if (clockCount == 33'd25000000)
                        begin
                            clockCount <= 33'b0;
                            outClk <= ~outClk;
                        end
                    else
                        begin
                            clockCount <= clockCount + 33'd1;
                        end
                end
            end
        end
endmodule

```

Testbench

```

`timescale 1ns / 100ps

module tb_clk_divider;

    reg inClk;
    reg reset;

    wire outClk;

    clk_divider uut (
        .inClk(inClk),
        .reset(reset),
        .outClk(outClk)
    );

    initial begin
        inClk = 0;
        forever #10 inClk = ~inClk;
    end
endmodule

```

```

    initial begin
        reset = 0;
        #100
        reset = 1;
        #100000000000
        $finish;
    end
end

```

```
endmodule
```

6 7-Segment Decoder Module

Code

```

module decoder( cntr ,Seven_Seg );
input  [2:0]  cntr;
output [7:0]  Seven_Seg;
reg  [6:0]  val;

```

```
assign Seven_Seg = {1'b1,~val};
```

```

always@( cntr )
begin
case( cntr )
3'd0: val = 7'b0111111;
3'd1: val = 7'b0000110;
3'd2: val = 7'b1011011;
3'd3: val = 7'b1001111;
3'd4: val = 7'b1100110;
3'd5: val = 7'b1101101;
3'd6: val = 7'b1111101;
3'd7: val = 7'b0000111;

```

```

endcase
end
endmodule

```

7 Top-level Code for 3-bit Johnson Counter Implementation on FPGA Board

Code

```

// Top level module

module johnson3bit(Seven_Seg, in_clk, rst, digit);

input  in_clk, rst;
output [7:0] Seven_Seg;
output [3:0] digit;
wire [2:0] cntr;
wire out_clk;

assign digit = 4'b0001;

johnson_counter jc0(cntr, out_clk, rst);
clk_divider clk0(in_clk, rst, out_clk);
decoder dec0(cntr,Seven_Seg);

```

endmodule

8 Constraints File

```
# Clock signal
set_property -dict { PACKAGE_PIN N11      IOSTANDARD LVCMOS33 } [get_ports { in_clk }];

# Switches
set_property -dict { PACKAGE_PIN L5      IOSTANDARD LVCMOS33 } [get_ports { rst }];#LSB

#7 segment display
set_property -dict { PACKAGE_PIN F2      IOSTANDARD LVCMOS33 } [get_ports { digit [0] }];
set_property -dict { PACKAGE_PIN E1      IOSTANDARD LVCMOS33 } [get_ports { digit [1] }];
set_property -dict { PACKAGE_PIN G5      IOSTANDARD LVCMOS33 } [get_ports { digit [2] }];
set_property -dict { PACKAGE_PIN G4      IOSTANDARD LVCMOS33 } [get_ports { digit [3] }]; #MSB

set_property -dict { PACKAGE_PIN G2      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [0] }];#A
set_property -dict { PACKAGE_PIN G1      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [1] }];#B
set_property -dict { PACKAGE_PIN H5      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [2] }];#C
set_property -dict { PACKAGE_PIN H4      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [3] }];#D
set_property -dict { PACKAGE_PIN J5      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [4] }];#E
set_property -dict { PACKAGE_PIN J4      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [5] }];#F
set_property -dict { PACKAGE_PIN H2      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [6] }];#G
set_property -dict { PACKAGE_PIN H1      IOSTANDARD LVCMOS33 } [get_ports { Seven_Seg [7] }];#DP
```

9 Errors and Corrections Made

1. **Error:** In the clock divider module, we had given active high reset and all others were active low resets, because of which there was no synchronization in the reset and display was not changing from 0.

Correction: Changed all the resets to active low.

2. **Error** (bit stream generation error) In the constraints file, we had given only one input pin for 7 segment display instead of 4 inputs for 4 bit digit.

Correction: Added 3 more package pins for digit.

10 Observations

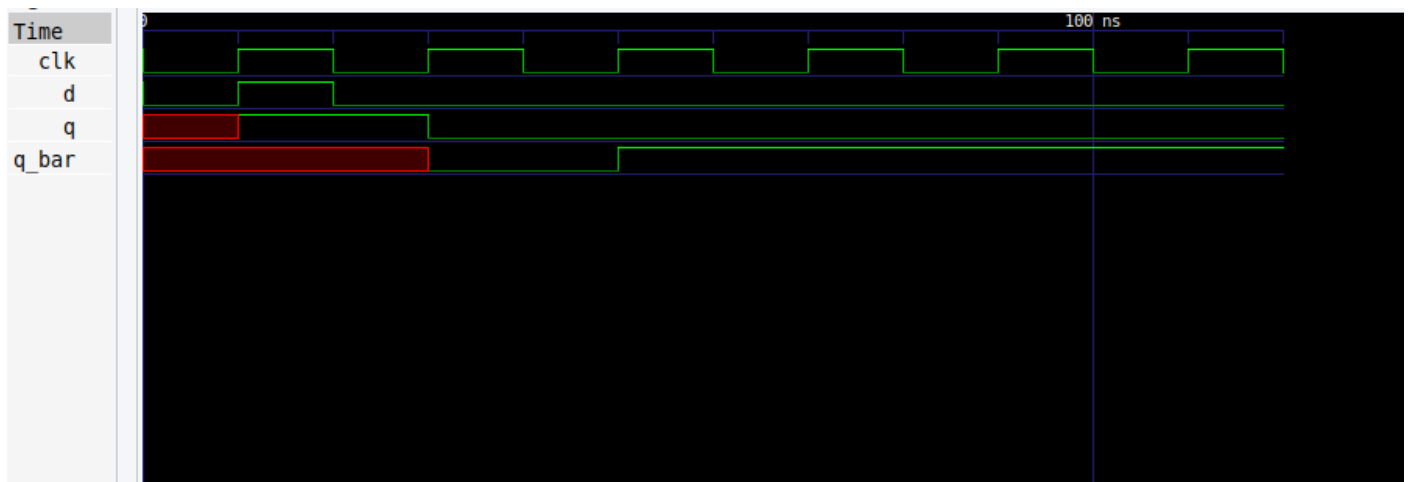


Figure 1: gtkwave of dff

 


Figure 2: gtkwave of dff with reset

 


Figure 3: gtkwave of johnson counter